

$$U_t = 15$$

$$U_{BE} = 0.6$$

$$U_z = 5.6$$

$$R_C = R_E = 100$$

Solve
$$[U_Z == U_{BE} + U_{RE}, U_{RE}]$$

$$\{\,\{\,\mathbb{U}_{\mathtt{RE}}\,\rightarrow\,5\,\boldsymbol{.}\,\,{}^{\backprime}\,\,\}\,\}$$

In[67]:=
$$I_E = \frac{U_{RE}}{R_E} = \frac{5}{100}$$

Out[67]=
$$\frac{1}{20}$$

In[73]:=
$$I_E = (1 + \beta) \times I_B$$

$$I_B = \frac{(1+\beta)}{I_E}$$

$$In[70]:= \mathbf{I_C} = \boldsymbol{\beta} \times \mathbf{I_B}$$

In[75]:=
$$I_{470} = \frac{U_t - U_z}{470}$$

Out[75]=
$$0.02$$

$$ln[76]:= I_Z = I_{470} - I_B$$

$$\ln[79] := \ \mathbf{U}_{CE} = \mathbf{U}_{t} - \mathbf{U}_{C} - \mathbf{U}_{E} = \mathbf{U}_{t} - \{\mathbf{I}_{C} \times \mathbf{R}_{C}\} - \{\mathbf{I}_{E} \times \mathbf{R}_{E}\} = \mathbf{15} - \mathbf{5.9} - \mathbf{5}$$

Out[79]=
$$4.1$$

$$ln[80]:= P_{470} = (I_{470})^2 \times 470$$

$$Out[80] = 0.188$$

In[81]:=
$$\mathbf{U}_{\mathbf{BC}} = \mathbf{U}_{\mathbf{BE}} - \mathbf{U}_{\mathbf{CE}}$$

$$Out[81] = -3.5$$